# SERIES AND PARALLEL CIRCUTS

Name_____ Date_____ #_____

**Series Circuit**: a circuit with ONE pathway

**Parallel Circuit**: a circuit with MORE THAN ONE pathway

Draw two different examples of each type of circuit below. Be sure to include **at least** 1 battery and 2 bulbs in each drawing.

## Series Circuit

## Series Circuit

What will happen in your series circuit if one bulb burns out?

_____

_____

## Parallel Circuit

## Parallel Circuit

What will happen in your parallel circuit if one bulb burns out?

_____

_____

© 2011 Lightbulb Minds, Inc.