SCHEMATIC DIAGRAMS

Name_____ #_____

Electricians and scientists use symbols to help make drawing a circuit easier. Here are some of the symbols you should know.

D-Cell	
Lamp	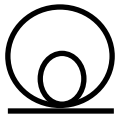 or
Wire	
Closed Switch	
Open Switch	
Motor	

Here is an example of a complete, closed circuit.

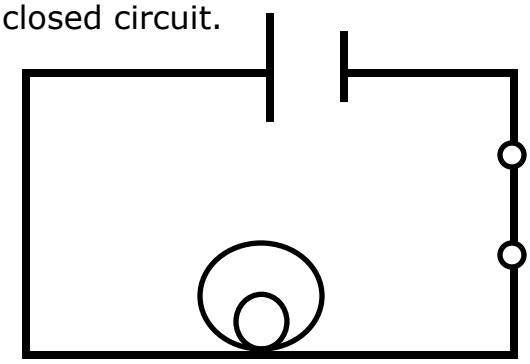

Draw a complete circuit with a motor and a switch.

Draw an open circuit with a motor and a lamp.

© 2011 Lightbulb Minds, Inc.